b)
$$X = \frac{v^2}{a} = \frac{220^2}{69.08} = \frac{700,63}{}$$

b)
$$C = \frac{1}{UV \cdot XC} = \frac{1000000}{314.700,63} = \frac{4.54}{54} \frac{VF}{F}$$

Tang de
$$\cos \theta = 0.55 = 1.518$$

Tony de $\cos \theta = 0.95 = -0.328$
 $\Delta + q = T_{g1} - T_{f2} = 1.19$

$$\Delta Q = P \cdot \Delta f_g = 46 \cdot 1.19 = 54,74 \text{ var}$$

c)
$$Xe = \frac{v^2}{100} = \frac{e20^2}{54,74} = 884,18 \Omega$$

c)
$$C = \frac{1}{W \cdot xc} = \frac{1000\,000}{314 \cdot 884,18} = \frac{3.6 \, \mu F}{3.6 \, xc}$$

Nº 11.1.2

a)
$$\cos \theta = \frac{P}{S} = \frac{140}{396} = \frac{0.35}{}$$

b)
$$Q = \sqrt{S^2 - P^2} = \sqrt{396^2 - 140^2} = 370,421 \text{ var}$$
 $tg \ de \ cos \ P \ 1 = > 0,35 = 2,646$
 $tg \ de \ cos \ P \ 2 = > 0,8 = -0,75$

$$\Delta + g = 1,896$$

$$\Delta Q = P \cdot \Delta f = 140 \cdot 1.896 = 256,44 \text{ var}$$

$$XC = \frac{U^2}{P} = \frac{220^2}{256,44} = 188,74 \Omega$$

c)
$$C = \frac{1}{W \cdot xc} = \frac{1 \cdot 10^6}{314 \cdot 188,74} = \frac{16,87}{16,87} = \frac{16,87}{16}$$

$$Afg = 2,162$$

11.1.2 Suite

$$Xc = \frac{U^2}{16} = \frac{220^2}{302,68} = 159,9 \Omega$$

Nº 11.1.3

$$tg de \cos \theta \approx -0.95 = -0.3296$$

$$Atg = 1.1508$$

$$Xc = \frac{U^2}{AR} = \frac{220^2}{2062,3N} = 23,468 \Omega$$

$$C = \frac{1.10^6}{\omega \cdot xc} = \frac{1.\cdot 10^6}{314 \cdot 23.46} = \frac{135,7 \ \mu F}{}$$

Nº 11. 1. 4

$$P_1 = \frac{P}{N} = \frac{1500}{0.73} = 2054, 8 \text{ W}$$

$$f_{q}$$
 de $\cos \theta_{2} = 0,91 = -0,4556$
 $\Delta f_{q} = 0,7135$

$$S = \frac{P}{\cos \varphi} = \frac{2054.8}{0.65} = 3161, 23 \text{ VA}$$

a)
$$Q = \sqrt{S^2 - P^2} = \sqrt{3161,23^2 - 2054,8^2} = \underline{9402,32} \, \sqrt{ar}$$

$$Q_{2} = P \cdot f_{2} = 2054,8 \cdot 0,4556 = \underline{936,16} \, \sqrt{ar}$$

$$\Delta Q = P \cdot \Delta f_{2} = 2054,8 \cdot 0,7135 = 1466,09 \, \sqrt{ar}$$

$$XC = U^2 = 220^2 - 33.013 \, \Omega$$

$$XC = \frac{U^2}{AR} = \frac{220^2}{1466,09} = 33,013 \Omega$$

b)
$$C = \frac{1.10^6}{\text{m} \cdot \text{xc}} = \frac{1.10^6}{314 \cdot 33,013} = \frac{96,47 \text{ MF}}{96,47 \text{ MF}}$$

11.1.4 Suite

c)
$$I_A = \frac{S}{u} = \frac{3161,23}{220} = \frac{14,37 \text{ A}}{220}$$

$$I_2 = \frac{S}{u} = \frac{2257,8}{220} = \frac{10,26 \text{ A}}{220}$$

Nº 11.1.5

$$S = \frac{P}{\cos \varphi} = \frac{170}{0,42} = 404,76 \text{ VA}$$

a)
$$Q = \sqrt{S^2 - P^2} = \sqrt{404,76^2 - 170^2} = \frac{367,33}{1007}$$

 $t_g de \cos P 1 = 0,42 = 2,1607$
 $t_g de \cos P 2 = 0,95 = -0,3286$
 $\Delta t_g = 1,8321$

$$AQ = P \cdot Afg = 170 \cdot 1.8321 = 3 M, 47 var$$

$$Yc = \frac{U^2}{AQ} = \frac{220^2}{311,47} = 155, 4 \Omega$$

$$C = \frac{1.10^6}{\text{w} \cdot \text{kc}} = \frac{1.10^6}{3/4.155,4} = \frac{20,5 \text{ pF}}{}$$

Nº 11. 1. 6

$$P = U \cdot I \cdot \cos 9 = 220 \cdot 14 \cdot 0,6 = 1848 W$$
 $fg de \cos 91 = 0,6 = 1,333$
 $fg de \cos 92 = 0,9 = -0,484$
 $Afg = 0,849$

$$AR = P \cdot Afg = 1848 \cdot 0,849 = 1568,97 \text{ var}$$

$$XC = \frac{U^2}{AR} = \frac{210^{2}}{1568,97} = 30,848 \cdot \Omega$$

$$C = \frac{1.10^6}{\text{W} \cdot \text{YC}} = \frac{1.10^6}{3/4 \cdot 30,848} = \frac{103,23 \text{ MF}}{}$$

Nº 11.1.7

$$S = U \cdot T = 220 \cdot 7, S = 1650 VA$$

$$Q = \sqrt{S^2 - P^2} = \sqrt{1650^2 - 1045^2} = 1276, 9 \text{ und}$$

M.1.7 Suite

a)
$$Cos P = \frac{P}{S} = \frac{1045}{1650} = \frac{0.65}{1650}$$

 $Xc = \frac{1}{w \cdot c} = \frac{1.106}{314.60} = 53,07 \Omega$

$$X_{C} = \frac{U^{2}}{AQ} = 7$$
 $AQ = \frac{U^{2}}{XC} = \frac{220U}{53,07} = 912 \text{ Var}$

$$\cos Q = \frac{P}{S} = \frac{1045}{1106,87} = \frac{0.944}{106,87}$$

$$S = \frac{P}{\cos \varphi} = \frac{22}{965} = 33,846 \text{ kVA}$$

$$S = \frac{P}{\cos \varphi} = \frac{22}{965} = 33,846^2 - 22^2 = 25,72 \text{ kvar}$$

$$t_{q} \text{ de } \cos \varphi = 1 = 9,65 = 1,169$$

$$t_{q} \text{ de } \cos \varphi = 1 = 9,65 = 1,169$$

$$t_{q} \text{ de } \cos \varphi = 1 = 9,85 = -9,75$$

$$\Delta t_{q} = \frac{9,22 \text{ kvar}}{2}$$

$$S = \frac{Q}{3} = \frac{9,22 \text{ kvar}}{3} = \frac{9,22 \text{ kvar}}{2} = \frac{14,499 \text{ kvar}}{2}$$

$$S = \frac{Q}{3} = \frac{9,22 \text{ kvar}}{3} = \frac{3,073 \text{ kvar}}{3} = \frac{169,85 \text{ var}}{2}$$

$$S = \frac{Q}{3} = \frac{1300}{2000} = \frac{9,65}{2000} = \frac{1519,85 \text{ var}}{2}$$

$$S = \frac{Q}{3} = \frac{120}{2000} = \frac{133,33}{2} = \frac{166,66 \text{ kVA}}{2}$$

$$S = \frac{P}{100} = \frac{120}{0.9} = \frac{133,33}{2} = \frac{166,66 \text{ kVA}}{2}$$

$$S = \frac{P}{100} = \frac{133,33}{2} = \frac{166,66 \text{ kVA}}{2}$$

$$S = \frac{P}{100} = \frac{133,33}{2} = \frac{166,66 \text{ kVA}}{2}$$

$$S = \frac{P}{100} = \frac{133,33}{2} = \frac{166,66 \text{ kVA}}{2}$$

$$S = \frac{P}{100} = \frac{133,33}{2} = \frac{166,66 \text{ kVA}}{2}$$

$$S = \frac{P}{100} = \frac{133,33}{2} = \frac{166,66 \text{ kVA}}{2}$$

$$S = \frac{P}{100} = \frac{133,33}{2} = \frac{166,66 \text{ kVA}}{2}$$

$$S = \frac{P}{100} = \frac{133,33}{2} = \frac{166,66 \text{ kVA}}{2}$$

$$S = \frac{P}{100} = \frac{133,33}{2} = \frac{166,66 \text{ kVA}}{2}$$

$$S = \frac{P}{100} = \frac{133,33}{2} = \frac{166,66 \text{ kVA}}{2}$$

$$S = \frac{P}{100} = \frac{133,33}{2} = \frac{166,66 \text{ kVA}}{2}$$

$$S = \frac{P}{100} = \frac{133,33}{2} = \frac{166,66 \text{ kVA}}{2}$$

$$S = \frac{P}{100} = \frac{133,33}{2} = \frac{166,66 \text{ kVA}}{2}$$

$$S = \frac{P}{100} = \frac{133,33}{2} = \frac{166,66 \text{ kVA}}{2}$$

$$S = \frac{1000 \text{ kvar}}{2} = \frac{1000 \text{ kvar}}{2}$$

$$S = \frac{1000 \text{ kvar}}{2} = \frac{1000 \text{ kvar}}{2}$$

$$S = \frac{1000 \text{ kvar}}{2} = \frac{1000 \text{ kvar}}{2}$$

$$\begin{array}{rcl}
 & A + g & = 0,4214 \\
c) & A Q = P \cdot A + g & = 183,38 \cdot 0,4214 & = \underline{56,186 \text{ kvav}} \\
a) & Q z = Q - AQ = 100 - 56,186 & = \underline{43,813 \text{ kvav}}
\end{array}$$

11. 2.3. Suite

$$J_{1} = \frac{P}{u \cdot v_{3} \cdot cos \, 9 \cdot n} = \frac{120000}{380 \cdot 1.73 \cdot 0.8 \cdot 0.9} = \frac{253.23 \, A}{253.23 \cdot 0.8}$$

b)
$$I_{2J} = \frac{P}{U \cdot \sqrt{3} \cdot \cos \theta \cdot n} = \frac{120000}{380 \cdot 1,73 \cdot 0,95 \cdot 0,9} = \frac{213,24 \text{ A}}{380 \cdot 1,73 \cdot 0,95 \cdot 0,9}$$

$$XC = \frac{U^2}{AR} = \frac{380^2}{50186} = 2,57 \Omega$$

c)
$$C = \frac{1.10^6}{W \cdot XC} = \frac{1.10^6}{314 \cdot 2.57} = \frac{1239 \text{ yF}}{}$$

Nº 11.2.4

a)
$$S = 0.7.73 = 380.28.1.73 = 18,407 \text{ kVA}$$
 $P = 4.7.73.6059 = 380.28.1.73.0,5735 = 10,556 \text{ kW}$
 $Q = 18^{2}-P^{2} = 18,407^{2}-10,556^{2} = 15,079 \text{ kvar}$
 $fg de \cos 9 = 0,5735 = 1,428$
 $fg de \cos 9 = 0,8 = 0,75$
 $1fg = 0,678$

b)
$$Q = Q_1 - \Delta Q = 15,079 - 7,161 = 7,917 kvar$$

$$P = 10,556 kW (ne change pas)$$

$$S = \sqrt{P^2 + Q^2} = \sqrt{10,556^2 + 7,917^2} = 13,195 kVA$$

e)
$$\bar{I} = \frac{1Q}{u \cdot \sqrt{3} \cdot \cos \varphi} = \frac{7161}{380 \cdot 1,73 \cdot 1} = \frac{10,13 \text{ A}}{10,13 \cdot 1}$$

$$\frac{N^{2} \text{ 11.2.5}}{P = \frac{W}{t} = \frac{2777}{21.8,25} = .16 \text{ kW}} \qquad \text{fg de } \cos 91 = 7.0,43 = 2,099}$$

$$\log \cot \cos 92 = 0,85 = 0,6197$$

$$\Delta + g = 1,479$$

Nº 11.2.6

$$tg de \cos \beta 1 => 0,3 = 3,179$$
 $tg de \cos \beta 2 => 0,82 = 0,698$

$$A fg = 2,481$$

b)
$$I = \frac{P}{U \cdot \sqrt{3} \cdot \omega_1 \rho} = \frac{350}{220 \cdot 1,73 \cdot 0.3} = \frac{3,0614}{200 \cdot 1,73 \cdot 0.3}$$

$$S = \frac{P}{\cos \varphi} = \frac{350}{0,82} = 426,8 \text{ VA}$$

$$I_{2} = \frac{S}{u \cdot I_{3}} = \frac{426.8}{120 \cdot 1.73} = \frac{1.12 A}{1.12 A}$$

c)
$$I condo = \frac{AQ}{U \cdot \sqrt{3}} = \frac{868.6}{220 \cdot 1.73} = \frac{2,279.A}{220 \cdot 1.73}$$

Nº 11.2.7

$$P = \frac{W}{t} = \frac{16200}{40.8} = 44,5 \text{ kW}$$

$$Q = \frac{W}{t} = \frac{17600}{40.5} = 55 \text{ kvar}$$

$$\cos \varphi = \frac{P}{S} = \frac{47.5}{72.67} = 0.653$$

$$f_{y} d + \cos \beta x = 0.7 = 0.75$$

$$\Delta f_{y} = 0.409$$

a)
$$AR = P \cdot Afg = 44,5 \cdot 0,409 = 19,466 kvar$$

 $R = R_1 - AR = 55 - 19,466 = 35,53 kvar$

Nº 11.2.8

a)
$$\cos \varphi = \frac{P}{S} = \frac{28}{46.4} = \frac{0,603}{}$$


11. 2. 8. 5aiteNella $S = \sqrt{P^2 + Q^2} = \sqrt{28^2 + 22^2} = 35,6 \text{ kVA}$ b) $\cos \varphi = \frac{P}{\text{polis}} = \frac{28}{35,6} = \frac{0.786}{35,6}$

 $C = \frac{1.10^{6}}{3} = \frac{1.10^{6}}{314.1014} = \frac{10,47 \text{ pF}}{3}$

b)
$$XC = \frac{U^2}{AQ} = \frac{380^2}{1784} = \frac{80,94 \Omega}{1784}$$
 $C = \frac{1.10^6}{U \cdot c} = \frac{1.10^6}{314 \cdot 80,94} = \frac{13, M}{3} = \frac{15, M}{3} = \frac{15,$

Courbes:

c)

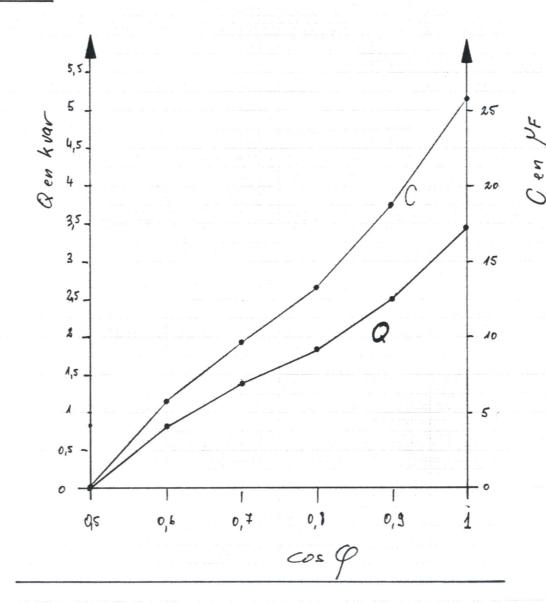

Nº 11. 2.10

$$S = \frac{P}{\cos \varphi} = \frac{130}{0.76} = 171.05 \text{ k VA}$$

$$Q = \left(\text{ne chang+ pos!} \right) = \sqrt{S^2 - P^2} = \sqrt{111.05^2 - 130^2} = 1111.17 \text{ k vor}$$

$$Nelle P = P_1 + P_2 = 130 + 50 = 180 \text{ kW}$$

$$Nelle S = \sqrt{P^2 + Q^2} = \sqrt{180^2 + 111.17^2} = 211.56 \text{ kVA}$$

$$Cos \varphi = \frac{N^{elle}P}{N^{elle}S} = \frac{180}{211.56} = \frac{0.851}{211.56}$$

Nº 11.2.11

$$P = P \cdot w \cdot 3 = 46 \cdot 16 \cdot 3 = 2208 \text{ W}$$

$$S = \frac{P}{\cos \varphi} = \frac{2208}{0,53} = 4166 \text{ VA}$$

$$f_{\varphi} \text{ de } \cos \varphi = 0,53 = 1,599$$

$$f_{\varphi} \text{ de } \cos \varphi = 0,95 = 0,8286$$

$$\Delta f_{\varphi} = 1,271$$

a)
$$AQ = P \cdot Afg = 2208 \cdot 1,271 = 2806 \text{ var}$$

 $XC = \frac{U^2}{AQ} = \frac{380^2}{2806} = 51,46 \Omega$

$$S$$
) $C = \frac{1.10^6}{U \cdot xc} = \frac{1.10^6}{3^{14} \cdot 51.46} = \frac{20.52}{9} = \frac{1.10^6}{3}$

Nº 11. 2. 12

$$P = \frac{W}{t} = \frac{160}{1} = 20 \text{ kW}$$

$$Q = \frac{W}{t} = \frac{216}{1} = 27 \text{ kvav}$$

$$S = \frac{P}{\cos \varphi} = \frac{20}{0.8} = 25 \text{ kVA}$$

$$Q = \frac{V}{\cos \varphi} = \frac{V}{0.8} = \sqrt{25^2 - 20^2} = 15 \text{ kvav}$$

$$\Delta Q = Q_1 - Q = 27 - 15 = 12 \text{ kvav}$$